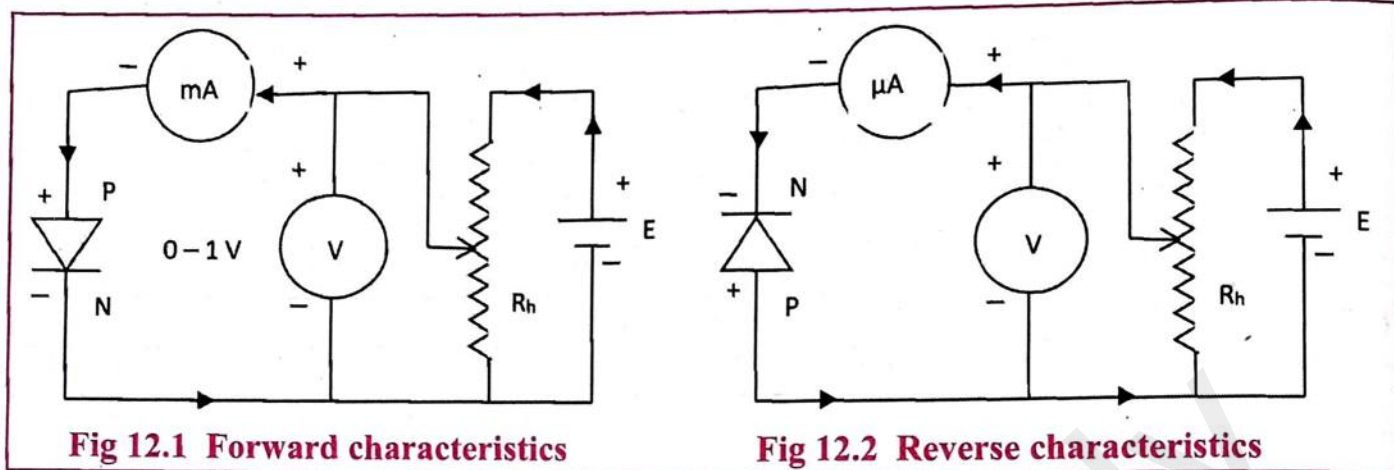


## EXPERIMENT NO. 12 DIODE CHARACTERISTICS

**Aim :** To draw the I-V characteristics curves of a P-N junction diode in forward and reverse bias.

**Apparatus :** D.C. power supply, Milliammeter (0-250mA), Microammeter, Voltmeter (0-5V, L.C. 0.1V), Silicon diode (IN4007) Rheostat, plug key and connecting wires.

**Circuit Diagram:**



**Observation:**

1. L.C. of Voltmeter: =  $0.05$  volt.
2. L.C. of Milliammeter: =  $0.2$  mA.
3. L.C. of Microammeter: =  $0.02$   $\mu$ A.

**Procedure :**

### A. Forward characteristics

1. Connect the circuit as shown in fig. 12.1
2. Voltage is increased from zero in steps of 0.1 V and corresponding current are recorded by the milliammeter.
3. For small value of the forward biased voltage (below 0.6 V), the forward biased current is zero. When applied voltage is less than  $V_k$ , a small current flows. Beyond  $V_k$ , a small increase in voltage produces a large increase in current.  $V_k$ , the voltage at which current start to increase rapidly, is called knee voltage or cut-in voltage. This voltage is equal to the barrier potential.
4. Plot the forward characteristics graph for diode (i.e. I-V curve) and find knee voltage  $V_k$ .
5. Calculate Static and dynamic resistance.

### B. Reverse characteristics

1. Connect the circuit as shown in fig. 12.2.
2. The reverse biased voltage is increased from zero in suitable steps and corresponding reverse biased current is measured by using microammeter.
3. As reverse voltage is increased from zero, reverse current increases and is equal to reverse saturation current ( $I_0$ ).
4. When reverse voltage is increased further, at a particular voltage, the current may increase rapidly. This is called breakdown voltage. When reverse voltage is less than breakdown voltage, the p-n junction diode offers a high resistance.
5. Plot the reverse biased characteristics graph for diode.

Observation table :


Forward Bias			Reverse Bias		
Obs. No.	Voltage (V)	Current (mA)	Obs. No.	Voltage (V)	Current ( $\mu$ A)
1	0.05	0	1	3	0.04
2	0.1	0	2	6	0.06
3	0.15	0	3	9	0.1
4	0.2	0	4	12	0.14
5	0.25	0	5	15	0.18
6	0.3	0	6	18	0.2
7	0.35	0	7	21	0.24
8	0.4	0.2	8	24	0.26
9	0.45	0.4	9	27	0.3
10	0.5	0.6	10	30	0.36
11	0.55	0.84	11	33	0.38
12	0.6	3.4	12	36	0.42
13	0.65	5.4	13	39	0.46
14	0.7	5.8	14	45	0.64
15	0.7	6.0	15	45	0.82

Calculations :

$$\text{Static resistance} = R_s = \frac{V}{I} = \frac{0.65}{5.4} = 0.1203 \Omega$$

$$\text{Dynamic resistance} = R_d = \frac{\Delta V}{\Delta I} = \frac{6}{0.06} = 0.01 \Omega$$

Graph:

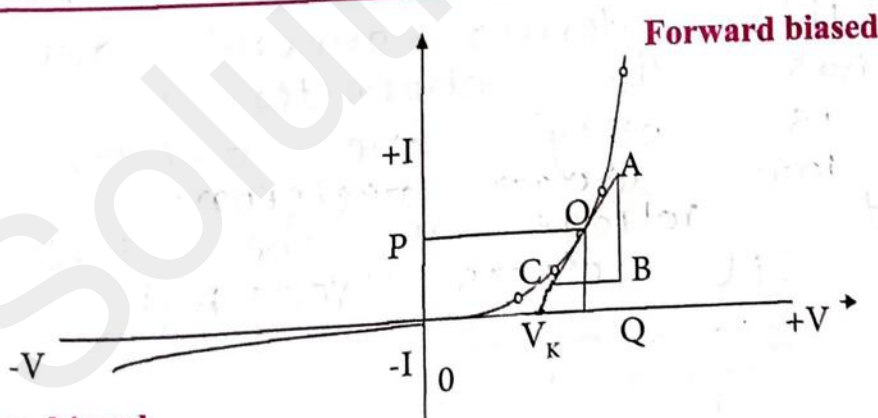

$$R_d = \frac{BC}{AB}$$

$$R_s = \frac{OQ}{OP}$$



### Result:

The forward and reverse characteristics of diode were studied.

1. Knee Voltage =  $V_K = 0.35$  volt.

2.  $R_d = 0.01 \Omega$ .

3.  $R_s = 0.1203 \Omega$ .

### Precautions:

1. Check the polarities of the milliammeter/ Microammeter/Ammeter/Voltmeter before passing current.
2. Use milliammeter/ Microammeter/Ammeter and voltmeter of proper least count.

### Additional Experiment you can do :

Determine voltage when Red, Yellow, green and blue LEDs, just start glowing (crossing knee voltage).

### Multiple Choice Question

1. The d.c. resistance of a diode is .....  
a) the same as it's a.c. resistance      b) more than as it's a.c. resistance  
✓ c) less than as it's a.c. resistance      d) zero
2. The knee voltage of a crystal diode is approximately equal to .....  
a) applied voltage      b) breakdown voltage  
c) forward voltage      d) barrier potential

### Questions

1. When is a junction diode said to be a) Forward biased b) reverse biased ?

① It is said to be forward biased when positive of battery is connected p-side and negative of battery is connected n-side.

② It is said the reverse based when positive terminals of battery is connected battery (n-side) to connect p-side.

2. When does a junction diode offer very high resistance? Why?

A p-n junction diode is one of the simplest this devices around and which has the characteristic of around is only one direction only low or near resistant is applied voltage as the diode whereas it offers very high.

Remark and sign of teacher: