


EXPERIMENT NO. 15

CHARACTERISTICS OF TRANSISTER

Aim : To study input and output characteristics of a common emitter NPN transistor.

Apparatus : Power supply, micro ammeter, mili-ammeter, voltmeter.

Circuit Diagram:

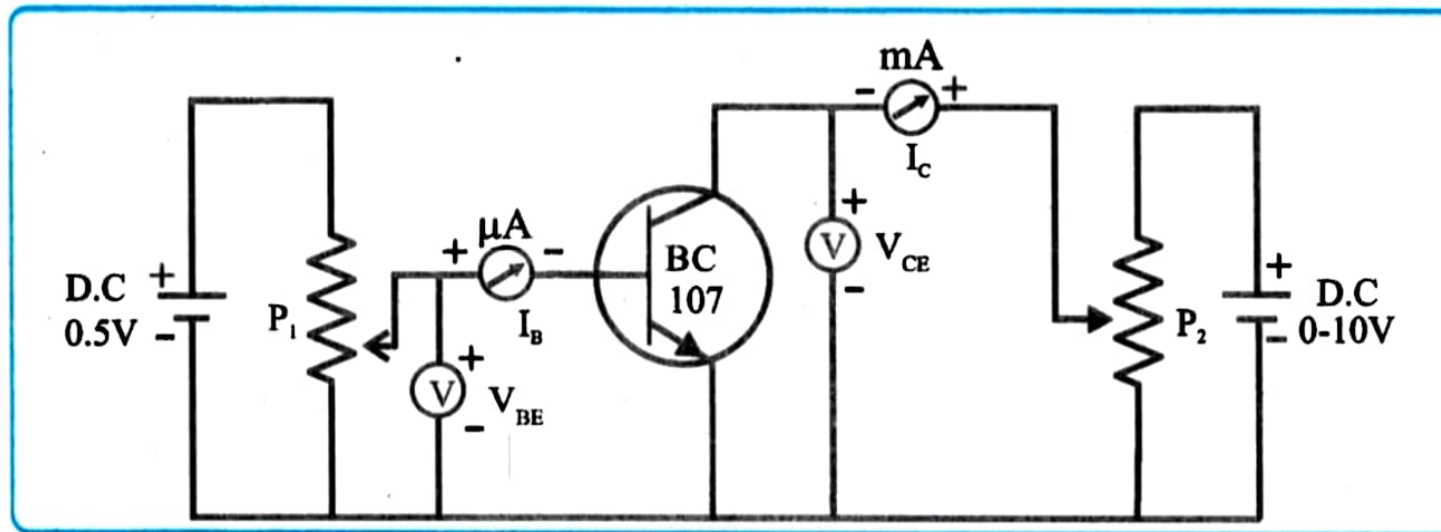

Components :

Observation Table : 1) Input Characteristics

Obs. No.	$V_{CE} = 5V$ at $I_B = 0$	
	$I_B (\mu A)$	$V_{BE} (V)$
1	0	0.2
2	0	0.3
3	0	0.4
4	0	0.5
5	15	0.6
6	140	0.7
7	10	1.75
8	20	4
9	30	5.5
10	40	7.5

2) Output Characteristics

Obs. No.	$I_B = 10 \mu A$		$I_B = 20 \mu A$		$I_B = 30 \mu A$	
	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$
1	1.5	0.1	2.75	0.1	3.5	0.1
2	3.75	0.2	6.25	0.2	8.75	0.2
3	3.75	0.3	7.5	0.3	10.5	0.3
4	3.75	0.4	7.5	0.4	10.75	0.4
5	3.75	0.5	7.5	0.5	10.75	0.5
6	3.75	0.6	7.5	0.6	10.75	0.6
7	3.75	0.7	7.5	0.7	10.75	0.7
8	3.75	0.8	7.5	0.8	10.75	0.8
9	3.75	0.9	7.5	0.9	10.75	0.9
10	3.75	1	7.5	1	10.75	1

Calculations :

From Output Characteristic graph.

1) For $I_B = 20 \mu A$

$I_C = \dots\dots 1.2 \dots mA$


2) Current amplification factor $\beta = I_C / I_B = \underline{6.50}$.

Graph :

1) Plot a graph of I_B against V_{BE} for input characteristic (Graph 1)



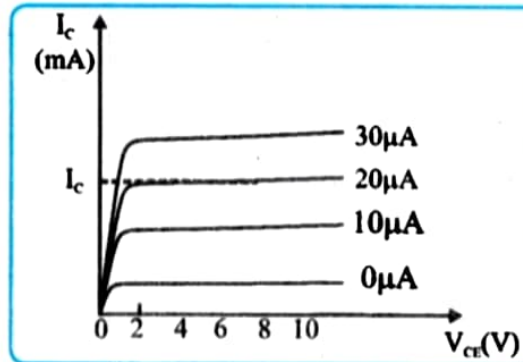2) Plot a graph of I_C against V_{CE} for output characteristic (Graph 2)



Conclusion :

The input characteristic is similar to the forward bias characteristic of PN junction diode.

Result : Current amplification factor $\beta = I_C / I_B = \underline{6.50}$


Questions

1. What do you mean by common emitter configuration ?


The configuration in which the emitter is connected between the collector and base is known as a common emitter configuration.

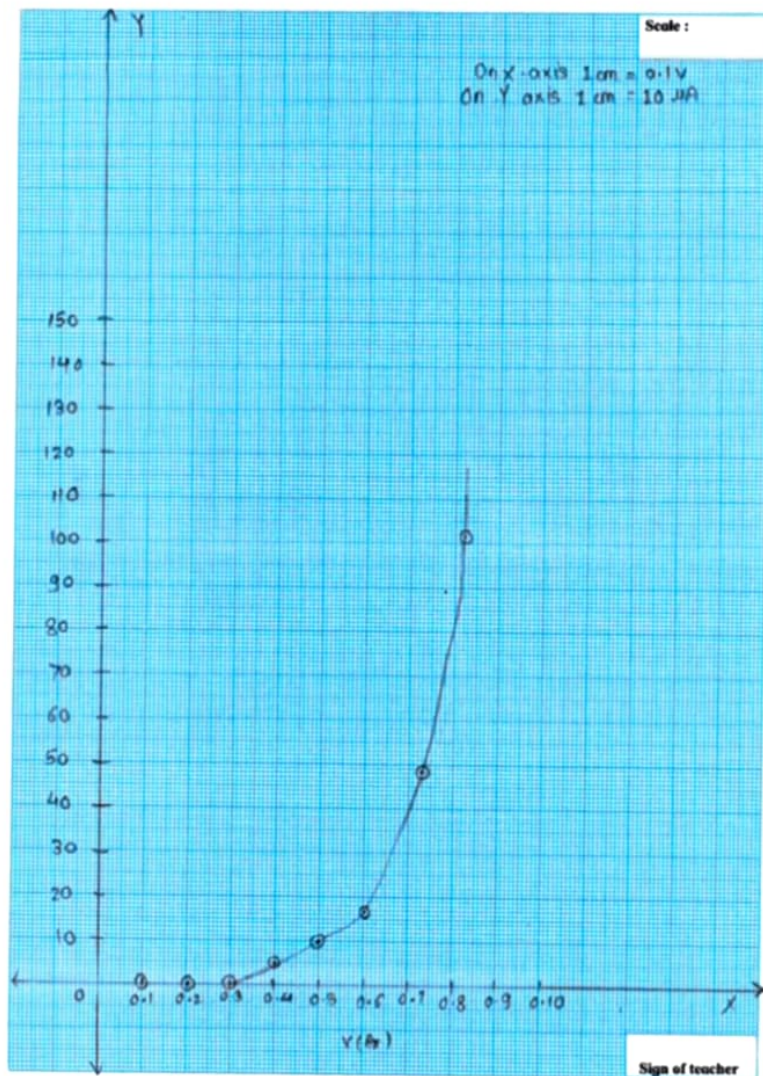2. How biasing is done for a transistor?

Transistor biasing can be achieved either by using a single feed back resistor or by using a simple voltage divider network to provide the required biasing voltage.



111

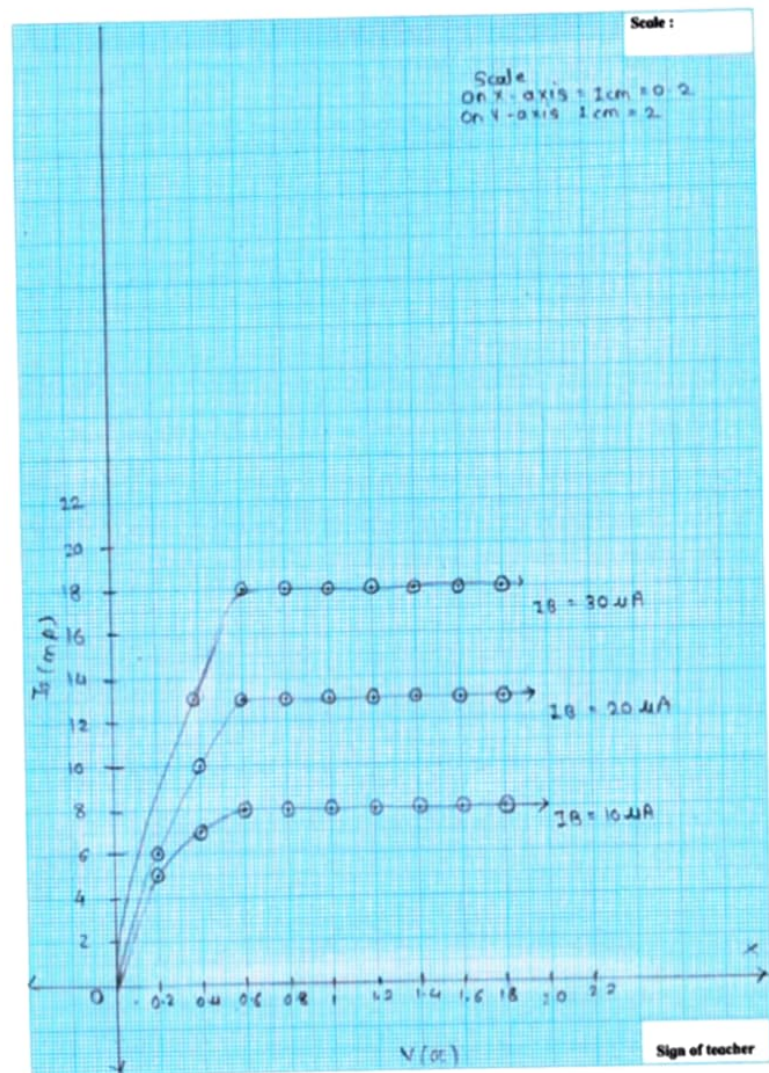

113